Centre Number			Candidate Number			For Exam	iner's Use
Surname							
Other Names						Examine	r's Initials
Candidate Signature							
						Question	Mark



General Certificate of Education Advanced Subsidiary Examination June 2010

Electronics

ELEC1

Unit 1 Introductory Electronics

Thursday 20 May 2010 9.00 am to 10.00 am

For this paper you must have:

- a pencil and ruler
- a calculator
- a Data Sheet.

Time allowed

1 hour

Instructions

- Use black ink or black ball-point pen.
- Fill in the boxes at the top of this page.
- Answer all questions.
- You must answer the questions in the spaces provided. Do not write outside the box around each page or on blank pages.
- Do all rough work in this book. Cross through any work you do not want to be marked.

Information

- The marks for questions are shown in brackets.
- The maximum mark for this paper is 67.

Examiner's Initials					
Question	Mark				
1					
2					
3					
4					
5					
6					
TOTAL					







2		A student designs an The fan should be sw certain levels that car	electronic system to con itched on only when bot n each be set independe	ntrol a ventilation f h the temperature ntly.	an for a greenhouse. and humidity exceed			
2	(a)	Choosing appropriate input, process and output subsystems from the list below, draw a labelled block diagram to show a possible design for the system.						
		Choose from:						
		AND gate	comparator	driver	humidity sensor			
		fan motor	temperature sensor	voltage divider				
					(7 marks)			
2	(b)	In which subsystem w	vould:					
2	(b) (i)	a MOSFET be used .			(1 mark)			
2	(b) (ii)	an on-amn be used			(T many			
	(6) (11)	an op-amp be used			(1 mark)			
2	(b) (iii)	a thermistor be used?	?		(d			
					(1 mark)			
2	(c)	The controller circuit operates from a 12V power supply and draws a current of 25 mA under all conditions.						
		The fan motor require same 12V power sup	es a current of 450 mA w ply.	hen switched on a	and operates from the			
		Calculate:						
2	(c) (i)	the total current draw	n by the whole system v	when the fan moto	r is switched on			
					(1 mark)			
2	(c) (ii)	the input power to the	e whole system when the	e fan motor is swit	ched on.			
					(2 marks)			



3 A student builds a quiz-scoring circuit that has five LEDs as its output. The student connects each of the five outputs of the circuit to the LEDs via five identical resistors as shown below.





3	(a) (v)	With no LEDs switched on, the quiz-scoring circuit alone draws 30 mA from the 9V power supply. Calculate the current consumption of this circuit with all the LEDs switched on.
3	(a) (vi)	Comment on the suitability of a small, low capacity 9V battery to power this system.
3	(b)	The student decides to economise on resistors by connecting all the LED anodes directly to the outputs of the circuit, and using a single resistor of the preferred value chosen in part (a)(iii) to connect all LED cathodes to 0V.
3	(b) (i)	Estimate the current through each active LED when three of them are switched on at the same time.
3	(b) (ii)	Describe the appearance of the LEDs as different numbers of them are switched on. Comment on the desirability of using a single resistor.
		(2 marks) Turn over for the next question



Turn over ▶









Turn over ▶

5 A butcher wants to fit an alarm to a deep freeze, which will warn him if there is a danger of damage to stock in the freezer. The freezer has sensors with the following outputs: T is logic 1 if the temperature is too high to store frozen food; and logic 0 if the temperature is at or below the required temperature C is logic 1 if the lid is closed and logic 0 if the lid is open. Т logic A system С A student is asked to produce a logic system to give an output A to operate the alarm (the alarm sounds if A is high). He decides that the alarm should sound if: the lid is closed and the temperature is too high, or the temperature is low and the lid is left open. He designs a system to implement this function. Write a Boolean expression for the 5 (a) output A, in terms of T and C. (3 marks)



5	(b)	Draw a logic diagram for the system, using any type of logic gates.
		(5 marks)
5	(C)	Using NAND gates only, draw a diagram of a logic system which has the same function as a 2-input OR gate.
		(2 marks)
5	(d)	Draw a logic diagram for the system in part (b), using NAND gates only. Draw a
		ring round any redundant gates or re-draw the final system.
		(5 marks)



Turn over ▶





6	(c)	What voltage would you expect from the output of this circuit when:	
6	(c) (i)	the temperature is 20 °C	(1 mark)
6	(c) (ii)	the temperature rises to 30 °C?	(1 mark)

(1 mark)

END OF QUESTIONS





